

Subject : Digital Computer Design & Computer Organization

Day : Monday
Date : 05/12/2016



Time : 02.00 PM TO 05.00 PM
Max Marks : 80 Total Pages : 1

N.B.:

- 1) Attempt **ANY FIVE** questions from Section – I and attempt **ANY TWO** questions from Section – II.
 - 2) Answers to both the sections should be written in the **SAME** answer book.
 - 3) Figures to the right indicate **FULL** marks.
-

SECTION – I

- Q.1** Explain 4 to 1 line Multiplexer using circuit diagram and truth table. [10]
- Q.2** Discuss the interrupt cycle with the help of flow chart. [10]
- Q.3** Discuss various types of flip flops with their merits and demerits. [10]
- Q.4** Explain different memory reference instructions. [10]
- Q.5** What is use of subroutines? Explain with example. [10]
- Q.6** Discuss the functioning of bidirectional shift register with parallel load with the help of circuit diagram. [10]
- Q.7** Write short notes on **ANY TWO** of the following: [10]
- a) Register transfer language
 - b) Assembler
 - c) Logic gates

SECTION – II

- Q.8** a) Write an assembly language program to find bigger number from 2 numbers. [10]
- b) Illustrate the need of memory organization. [05]
- Q.9** a) Simplify the following using K-map: [10]
- i) $F(A, B, C) = \sum (1, 2, 3, 6, 7)$
 - ii) $F(A, B, C, D) = \sum (0, 2, 3, 4, 5, 6, 7, 8, 10, 13, 15)$
- b) Using De-Morgan's theorem show that: [05]
- $$A + A'B + A'B' = 1.$$
- Q.10** What is sequential circuit? Explain the structure of sequential circuit with the help of appropriate circuit diagram and state table. [15]

* * * *